



*Design, simulation and analysis (dc and small signal) of
Common-Source Amplifier
for transconductance (g_m) of 20 mS.*

Submitted By

KUNAL KAUSHIK

21307R020

M.Tech. SSD

OBJECTIVE

The objective of this assignment is to design the common source amplifier for **transconductance (g_m) of 20 mS** and analyse the circuit with dc analysis and small signal analysis.

The analysis is done in two parts:

1. DC ANALYSIS:

This analysis is done with different plots of following DC parameters.


- $\log_{10}(I_D)$ Vs. V_{GS}
- $\log_{10}(I_D/W)$ Vs. g_m/I_D
- $\log_{10}(f_T)$ Vs. g_m/I_D

2. AC ANALYSIS


- By fixing V_{GS} and W , varying I_D
- By fixing W and I_D , varying V_{GS}
- By fixing I_D and V_{GS} , varying W

INTRODUCTION TO COMMON SOURCE AMPLIFIER

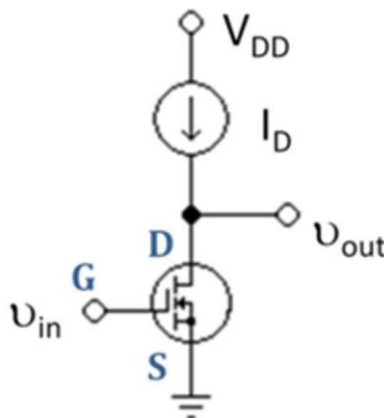The most used MOS-small signal amplifier that we have is the common source (CS) amplifier.



➤ DC ANALYSIS

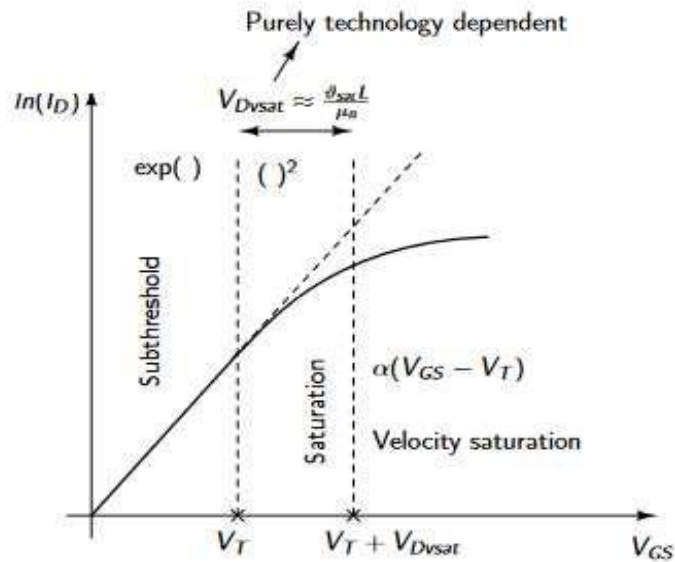

Plot for $\log_{10}(I_D)$ Vs. V_{GS}

$$I_D = \begin{cases} 0 & \forall V_{GS} \leq V_T \\ \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_T) V_{Dmin} - \frac{V_{Dmin}^2}{2} \right] (1 + \lambda V_{DS}) & \forall V_{GS} > V_T \end{cases}$$

where $V_{Dmin} = \text{minimum of } \{V_{DS}, (V_{GS} - V_T), V_{Dsat}\}$.

- Above expression is valid for linear, saturation and velocity saturation regions.

➤ **SMALL SIGNAL ANALYSIS**

- The gain of the amplifier is defined as

$$\text{Gain} = g_m r_o$$

- The transconductance (g_m) is defined as

$$\begin{aligned} g_m &= \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \\ &= \left(2I_D \mu_n C_{ox} \frac{W}{L} \right)^{1/2} \\ &= (2I_D) / (V_{GS} - V_{TH}) \end{aligned}$$

- The Bandwidth is defined as

$$BW = 1/(2\pi r_o C_L)$$

The variation of I_D , W and V_{GS} is governed by the equation,

$$g_m r_o = \frac{1}{\lambda} \frac{g_m}{I_D} = \frac{2}{V_{GS} - V_{TH}}$$


&

$$GBW = \frac{g_m}{2\pi C_0}$$

OBSERVATIONS AND CALCULATIONS



- DC ANALYSIS

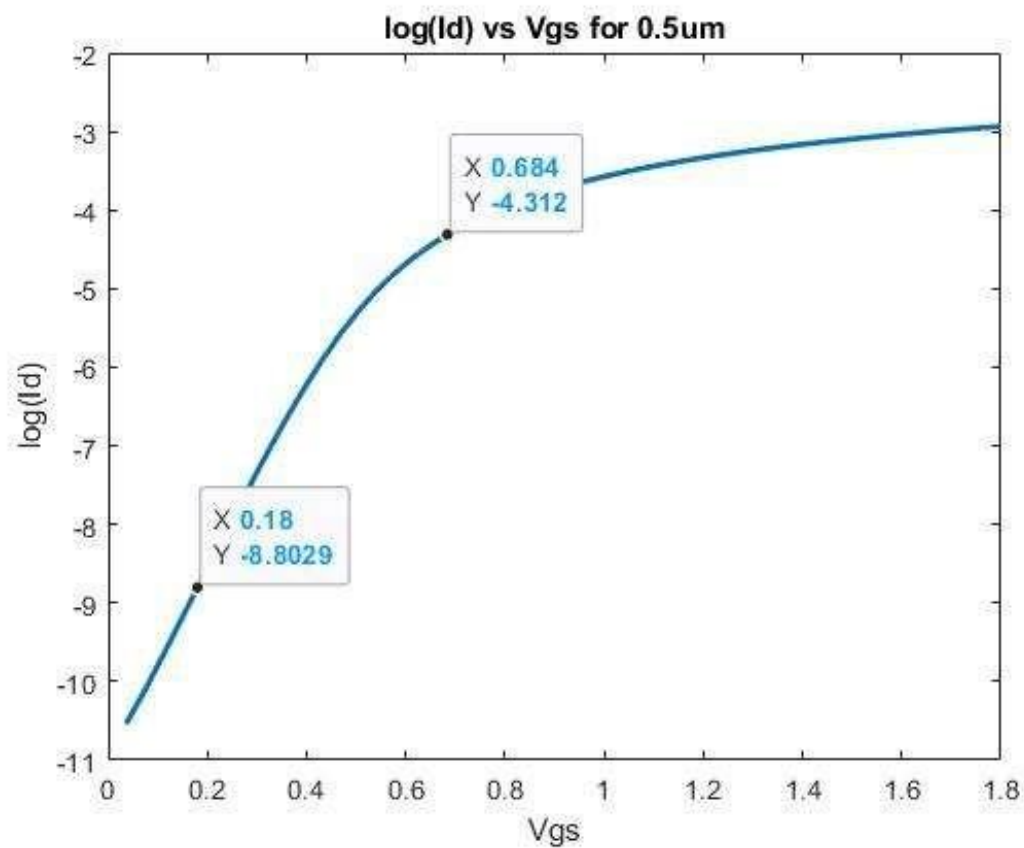1. For $V_{GS} = 1.8V$ and $V_{DS} = 1.8V$
W = 0.5 μm and **L = 4.2 μm**




Weak Inversion starts from $V_{GS} = 0.18 V$ to $V_{GS} = 0.684 V$

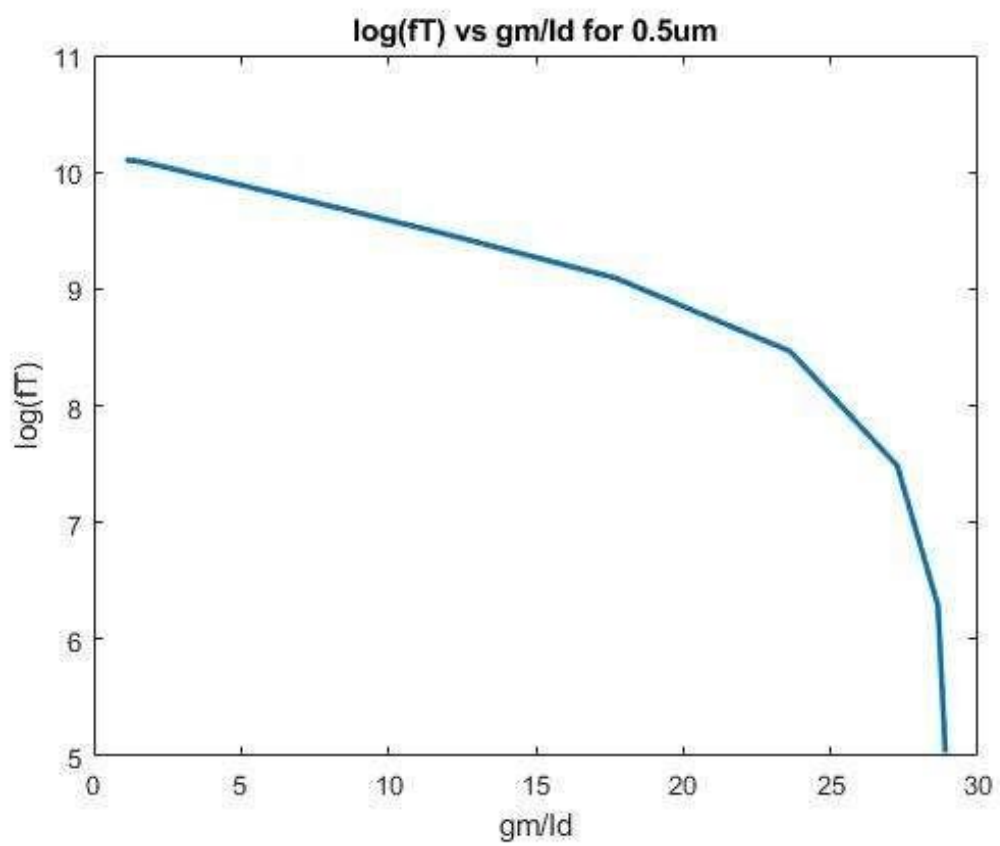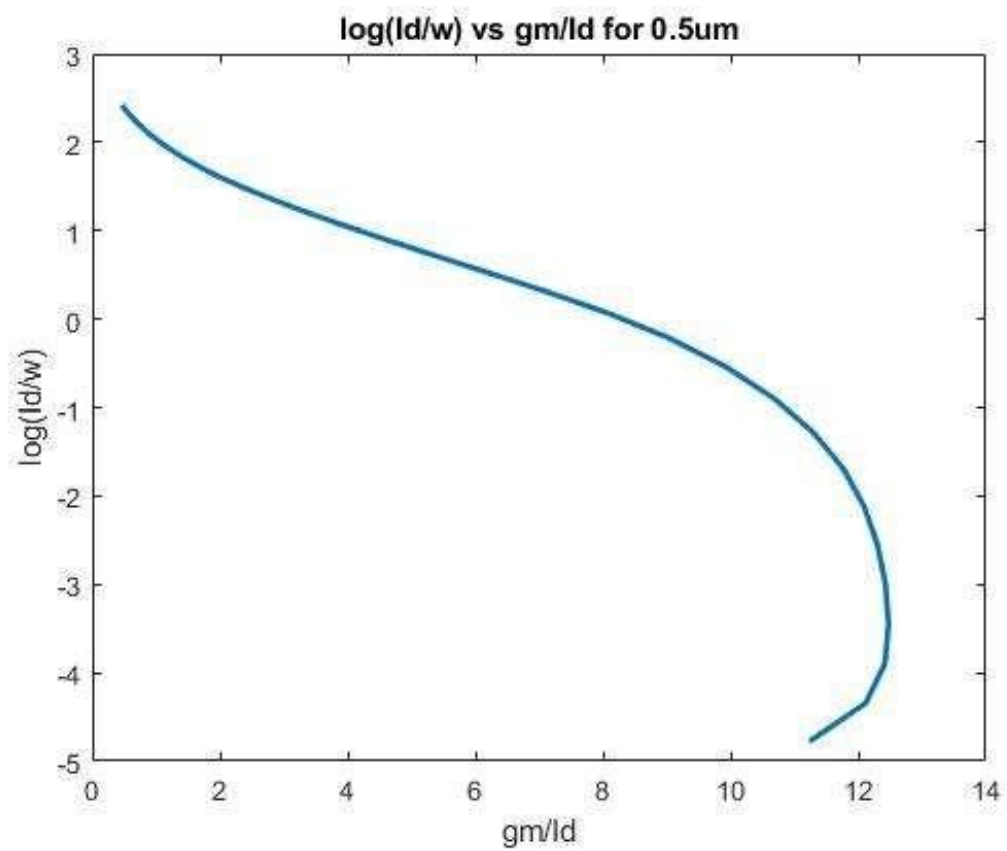Strong Inversion starts from $V_{GS} = 0.684 V$




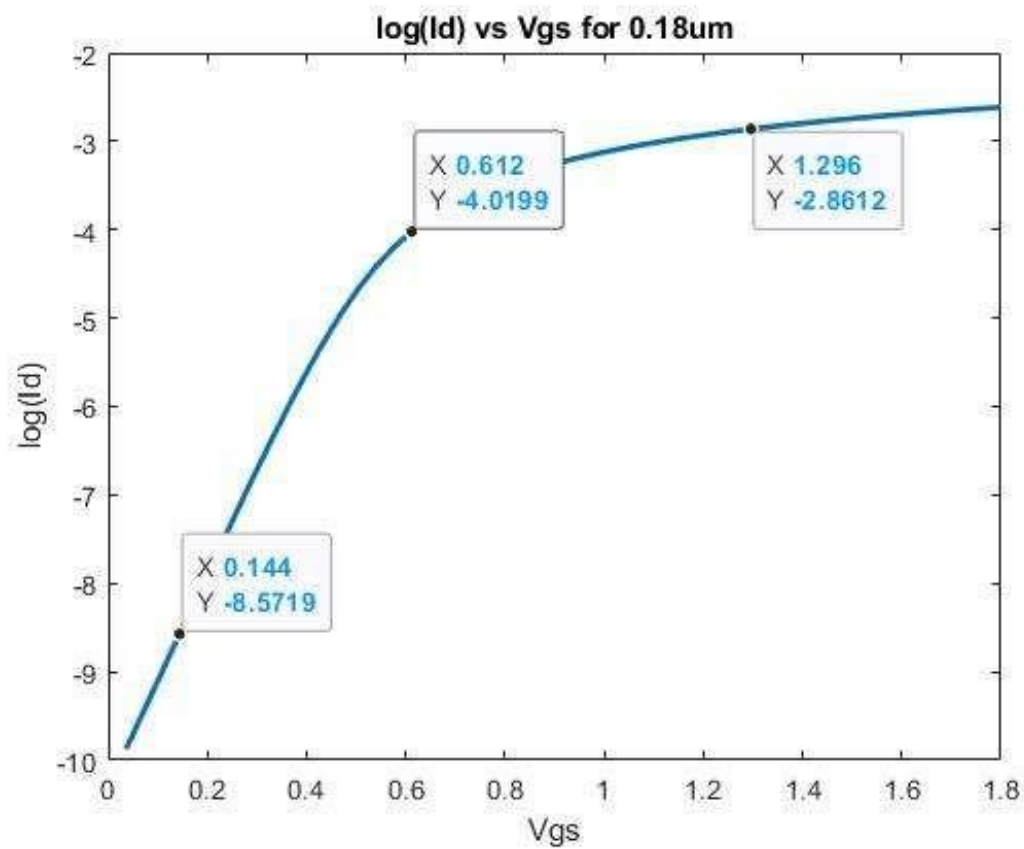
2. For $V_{GS} = 1.8V$ and $V_{DS} = 1.8V$
 $W = 0.18 \mu m$ and $L = 4.2 \mu m$



Weak Inversion starts from $V_{GS} = 0.144 V$ to $V_{GS} = 0.612 V$

Strong Inversion starts from $V_{GS} = 0.612 V$ to $V_{GS} = 1.296 V$

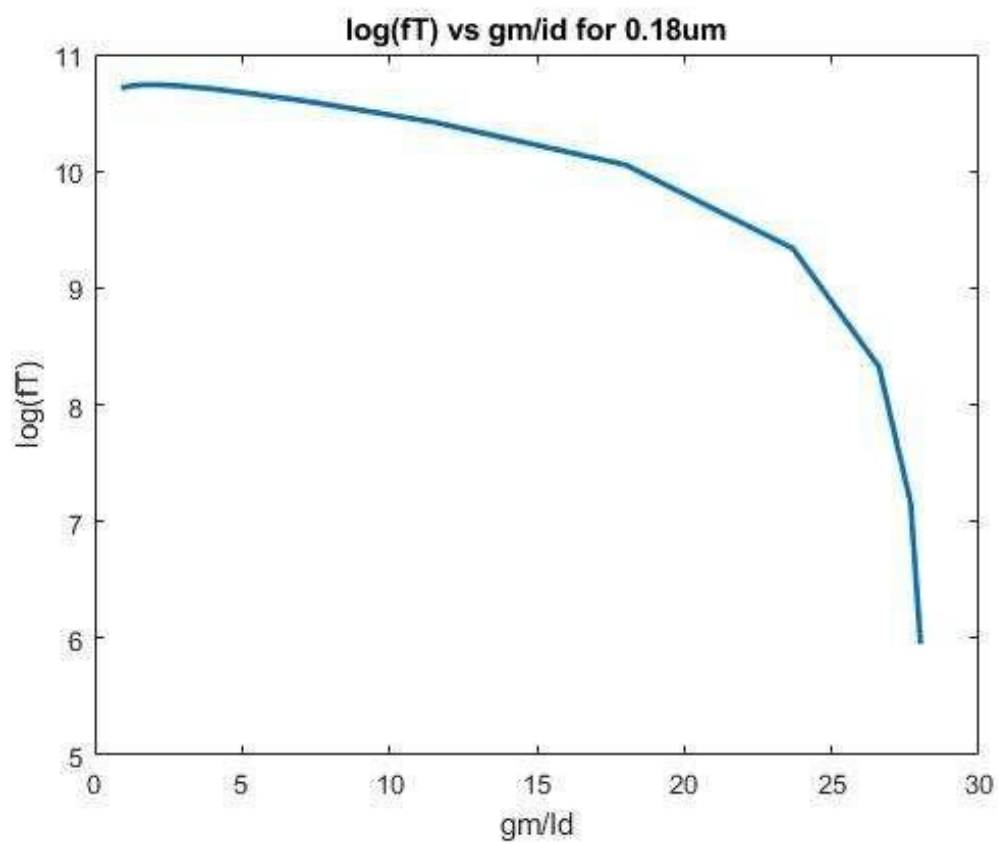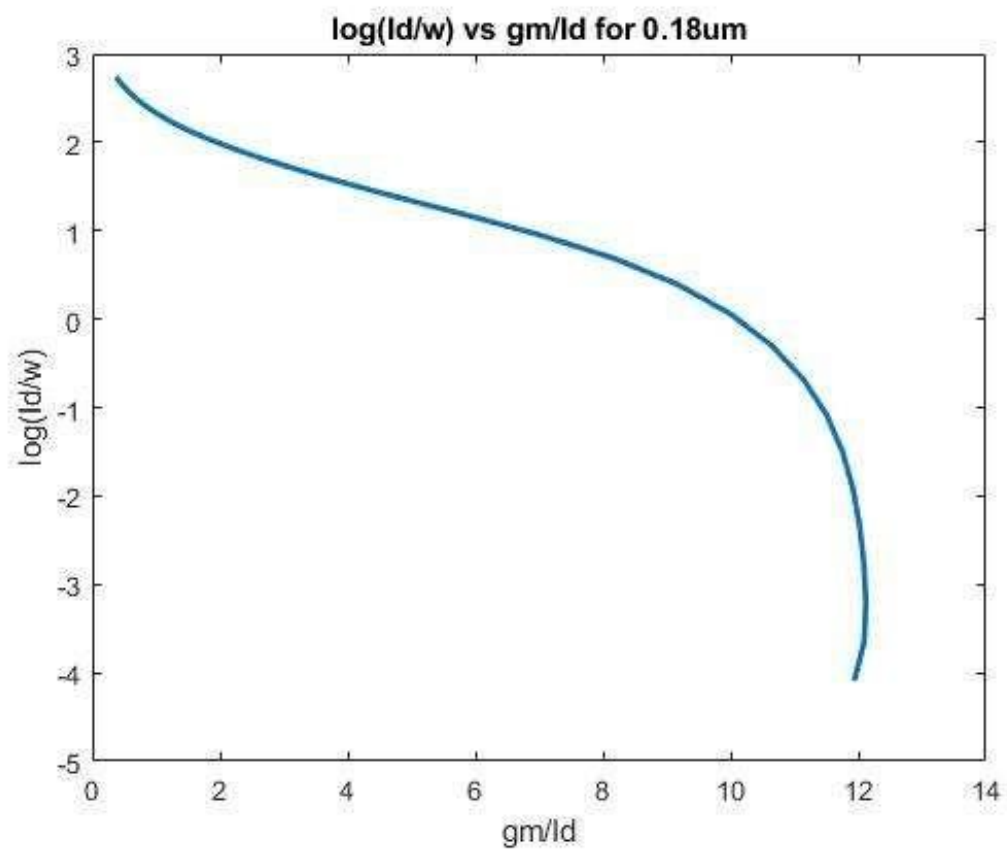
Velocity Saturation starts from $V_{GS} = 1.296 V$



- **SMALL SIGNAL ANALYSIS**

1. For $V_{GS} = 0.640 \text{ V}$ and $W = 23 \times 4.2 \text{ } \mu\text{m} = 96.6 \text{ } \mu\text{m}$

By varying I_D , we get

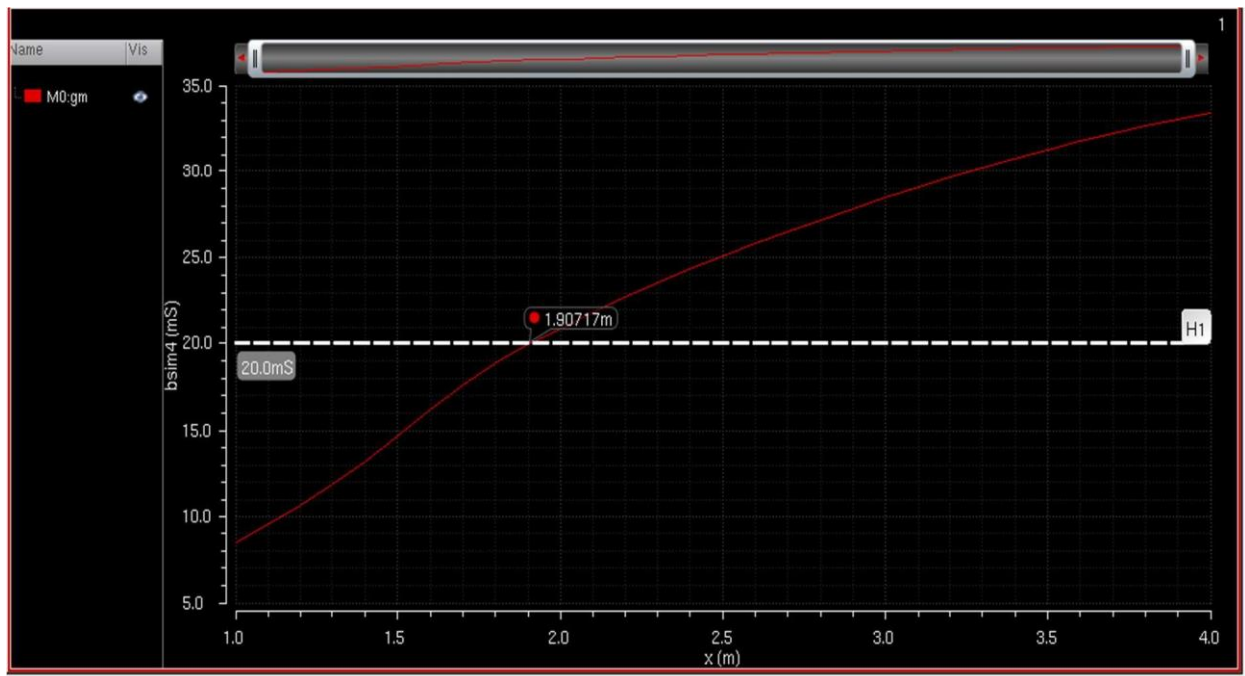


At $g_m = 20 \text{ mS}$,

$I_D = 1.90717 \text{ mA}$ and

$$\frac{g_m}{I_D} = 10.5$$

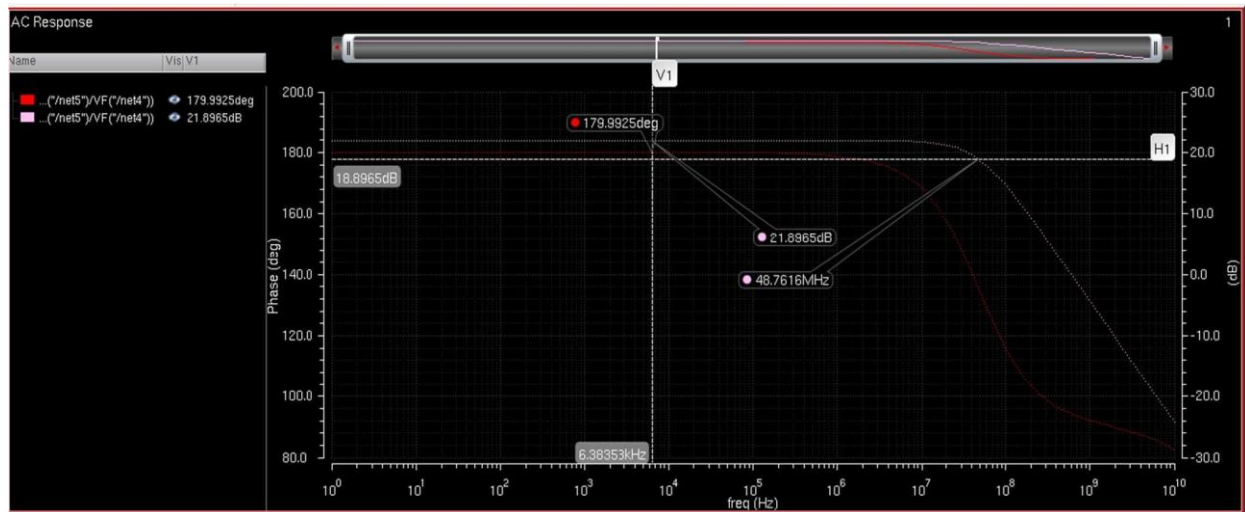a. GAIN

For $I_D = 1.90717 \text{ mA}$ and $v_{in} = 5 \text{ mV}$ (Small signal sinusoidal)



$$\begin{aligned} \text{Gain} &= g_m r_o = 21.8965 \text{ dB} \\ &= 12.44 \end{aligned}$$

b. BANDWIDTH

BW = 48.7616 MHz (After Simulation)

$$r_o = \frac{\text{Gain}}{g_m} = 622.2 \Omega$$

$$\text{Calculated BW} = 1/(2\pi r_o C_L) = 51.175 \text{ MHz}$$

c. POWER

$$\begin{aligned} \text{Power} &= I_D^2 r_o \\ &= (1.90717 \text{ mA})^2 (622.2 \Omega) \\ &= 2.263 \text{ mW} \end{aligned}$$

d. AREA

$$\begin{aligned} \text{Area} &= WL \\ &= (96.6 \mu\text{m})(4.2 \mu\text{m}) \\ &= 405.72 \times 10^{-12} \text{ m}^2 \end{aligned}$$

e. LINEARITY

The magnitude of first and third harmonics in DFT analysis for 50 KHz is observed in the following plot:




Harmonic distortion due to third harmonic component is given by


$$\begin{aligned} \text{HD}_3 &= \frac{\text{Third Harmonic Component}}{\text{First Harmonic Component}} \\ &= \frac{1.948659}{13.81216} = 0.14108 = 14.108 \% \end{aligned}$$

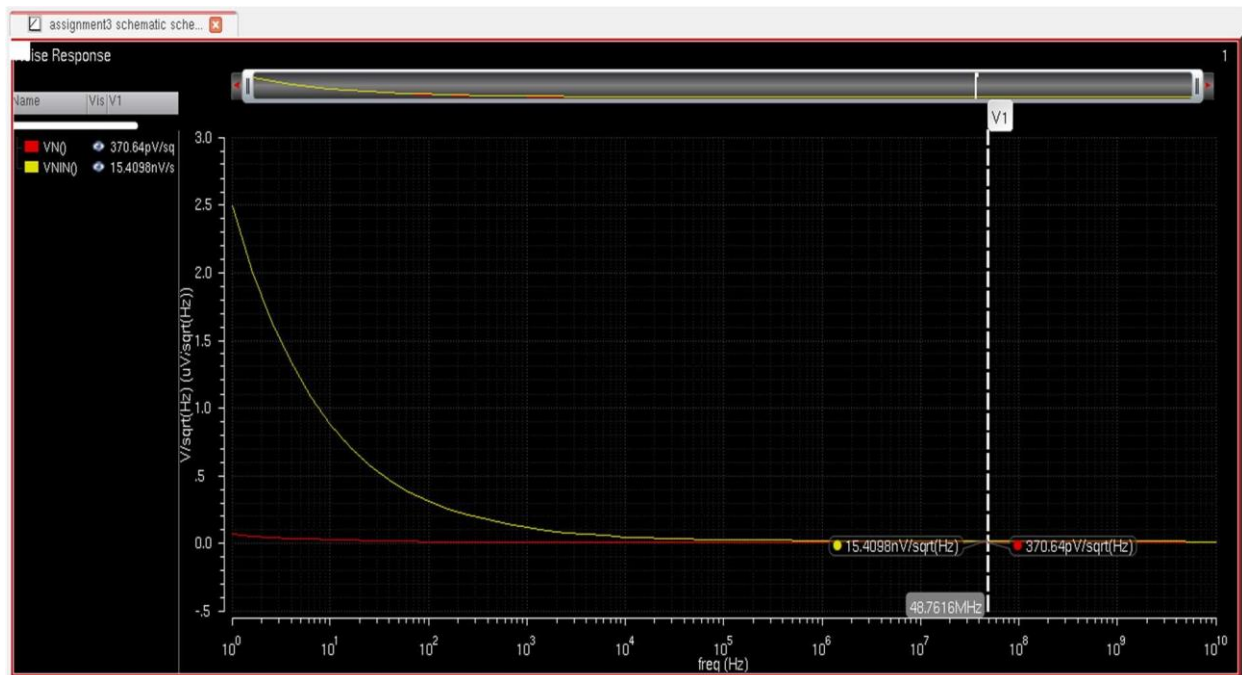f. NOISE

Input and output Noise is simulated in the following plot



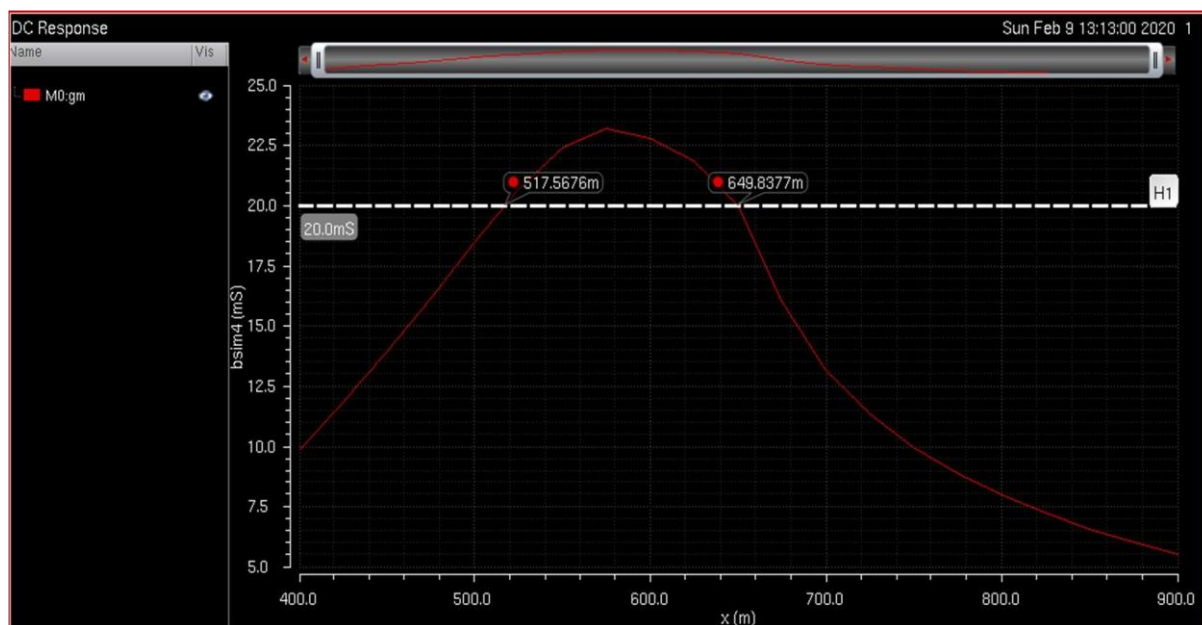- For $I_D = 2 \text{ mA}$ and $W = 23 \times 4.2 \text{ } \mu\text{m} = 96.6 \text{ } \mu\text{m}$
By varying V_{GS} , we get




At $g_m = 20 \text{ mS}$,

$V_{GS} = 0.64983 \text{ V}$ and

$$\frac{gm}{ID} = 10$$

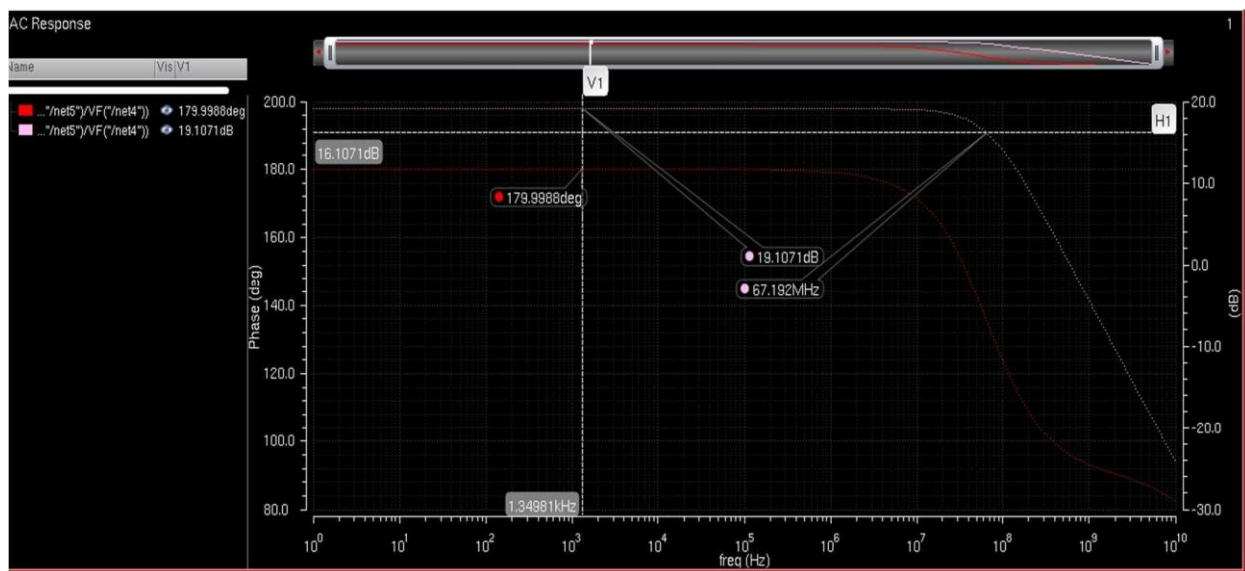a. GAIN

For $V_{GS} = 0.64983 \text{ V}$ and $v_{in} = 5 \text{ mV}$ (Small signal sinusoidal)



$$\begin{aligned} \text{Gain} &= g_m r_o = 19.1071 \text{ dB} \\ &= 9.023 \end{aligned}$$

b. BANDWIDTH

$BW = 67.192 \text{ MHz}$ (After Simulation)

$$r_o = \frac{\text{Gain}}{g_m} = 451.15 \Omega$$

$$\text{Calculated BW} = 1/(2\pi r_o C_L) = 70.554 \text{ MHz}$$

c. POWER


$$\begin{aligned} \text{Power} &= I_D^2 r_o \\ &= (2 \text{ mA})^2 (451.15 \Omega) \\ &= 1.8046 \text{ mW} \end{aligned}$$

d. AREA

$$\begin{aligned} \text{Area} &= WL \\ &= (96.6 \mu\text{m})(4.2 \mu\text{m}) \\ &= 405.72 \times 10^{-12} \text{ m}^2 \end{aligned}$$

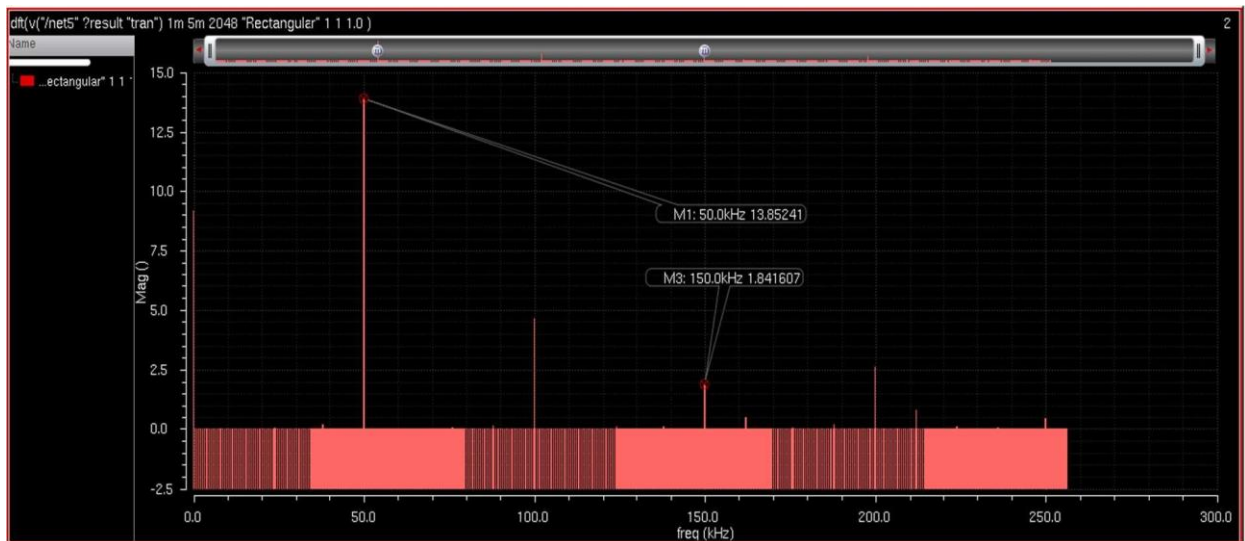e. LINEARITY

The magnitude of first and third harmonics in DFT analysis for 50 KHz is observed in the following plot:




Harmonic distortion due to third harmonic component is given by


$$\begin{aligned} \text{HD}_3 &= \frac{\text{Third Harmonic Component}}{\text{First Harmonic Component}} \\ &= \frac{1.841607}{13.85241} = 0.132944 = 13.29 \% \end{aligned}$$

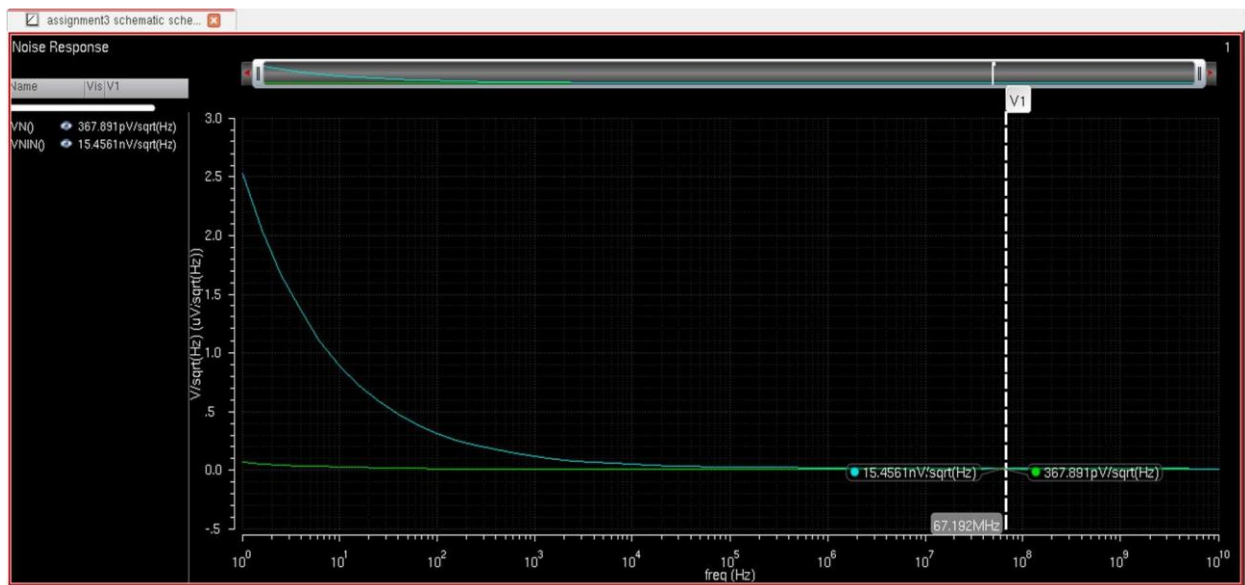f. NOISE

Input and output Noise is simulated in the following plot



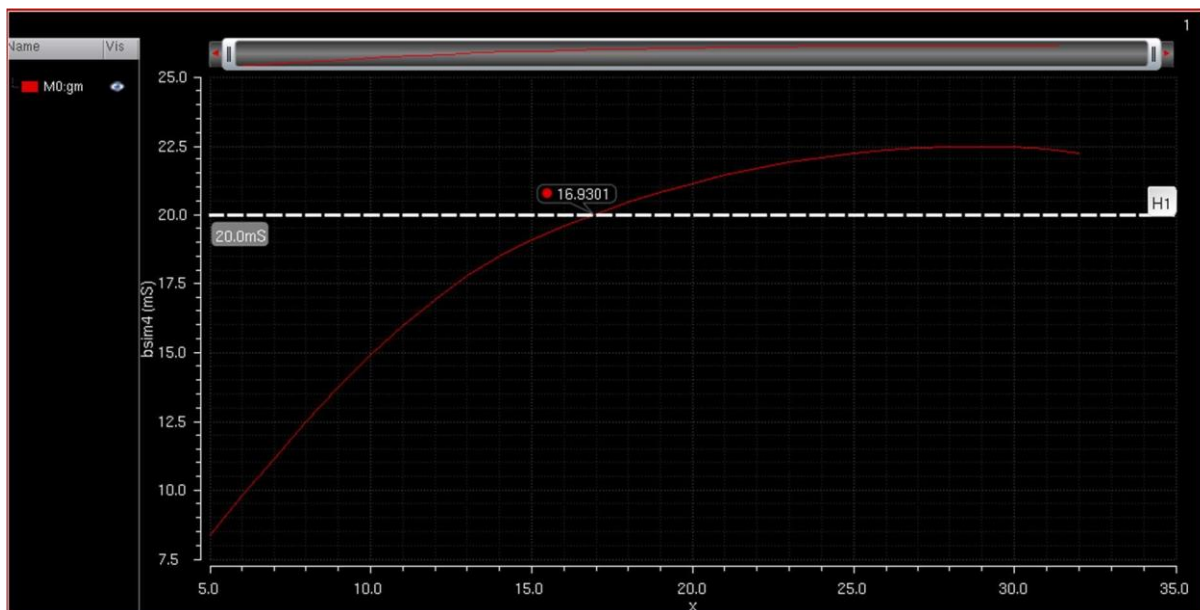3. For $I_D = 2 \text{ mA}$ and $V_{GS} = 0.625 \text{ V}$
By varying W , we get




At $g_m = 20 \text{ mS}$,

$$W = (16.9301 \sim 17) \times (4.2 \text{ } \mu\text{m}) = 71.4 \text{ } \mu\text{m}, \text{ and}$$

$$\frac{g_m}{I_D} = 10.01$$

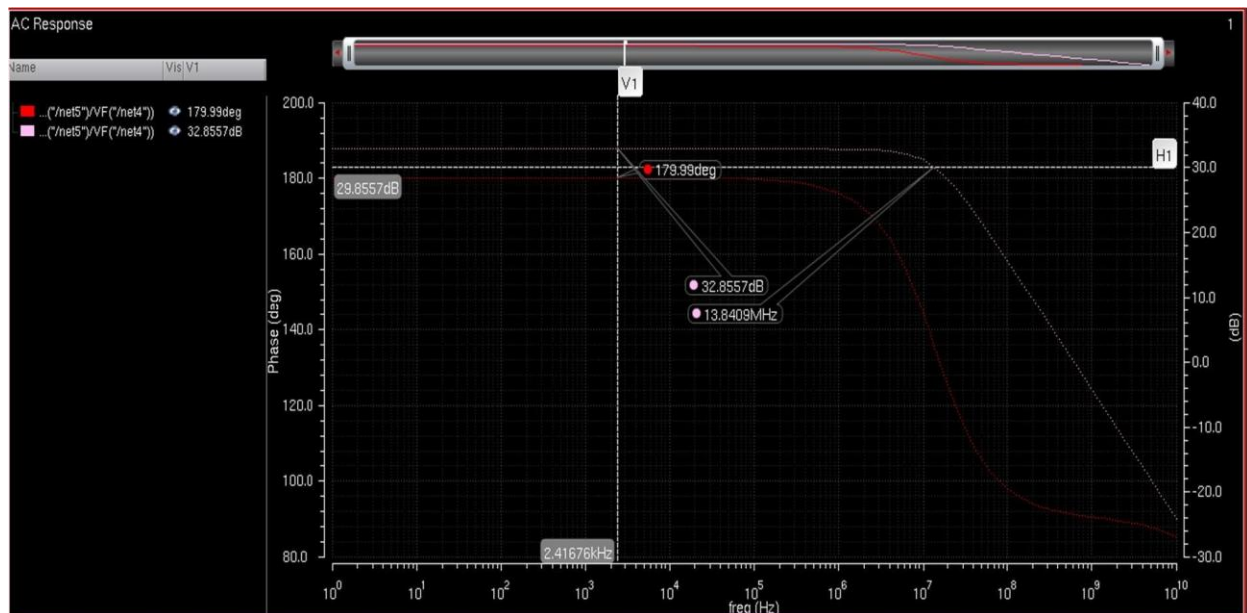a. GAIN

For $V_{GS} = 0.64983 \text{ V}$ and $v_{in} = 5 \text{ mV}$ (Small signal sinusoidal)



$$\text{Gain} = g_m r_o = 32.8557 \text{ dB}$$

$$= 43.932$$

b. BANDWIDTH

$$\text{BW} = 13.8409 \text{ MHz (After Simulation)}$$

$$r_o = \frac{\text{Gain}}{g_m} = 2196.6 \text{ } \Omega = 2.1966 \text{ K}\Omega$$

$$\text{Calculated BW} = 1/(2\pi r_o C_L) = 14.491 \text{ MHz}$$

c. POWER


$$\begin{aligned} \text{Power} &= I_D^2 r_o \\ &= (2 \text{ mA})^2 (2196.6 \Omega) \\ &= 8.786 \text{ mW} \end{aligned}$$

d. AREA

$$\begin{aligned} \text{Area} &= WL \\ &= (71.4 \mu\text{m})(4.2 \mu\text{m}) \\ &= 299.8 \times 10^{-12} \text{ m}^2 \end{aligned}$$

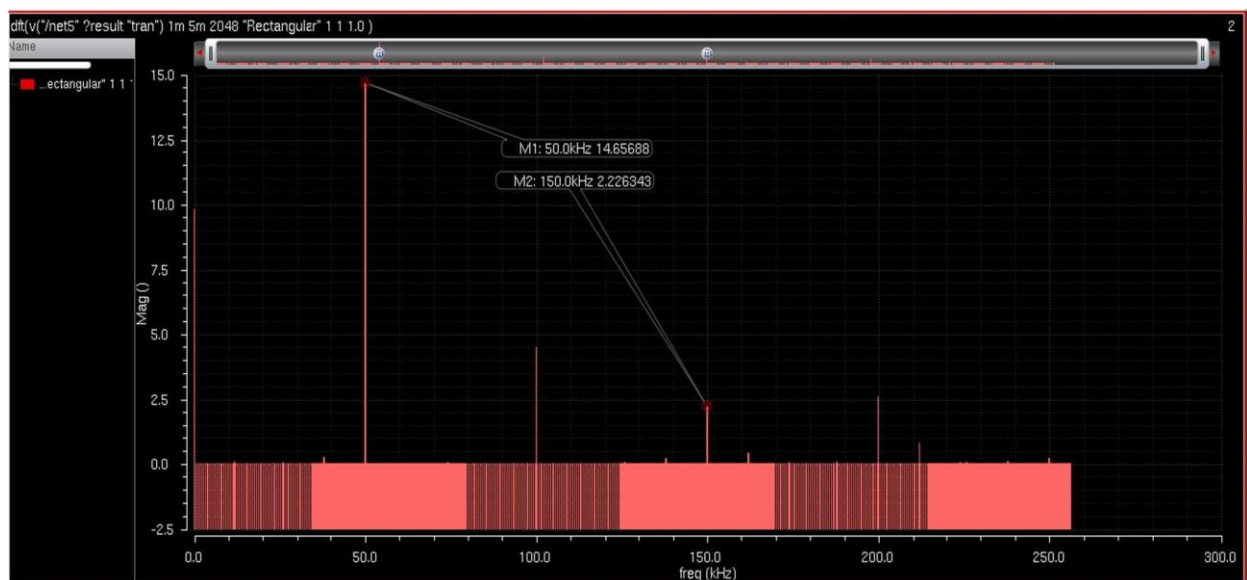e. LINEARITY

The magnitude of first and third harmonics in DFT analysis for 50 KHz is observed in the following plot:




Harmonic distortion due to third harmonic component is given by

$$\text{HD}_3 = \frac{\text{Third Harmonic Component}}{\text{First Harmonic Component}}$$

$$= \frac{2.226343}{14.65688} = 0.151897 = 15.18 \%$$

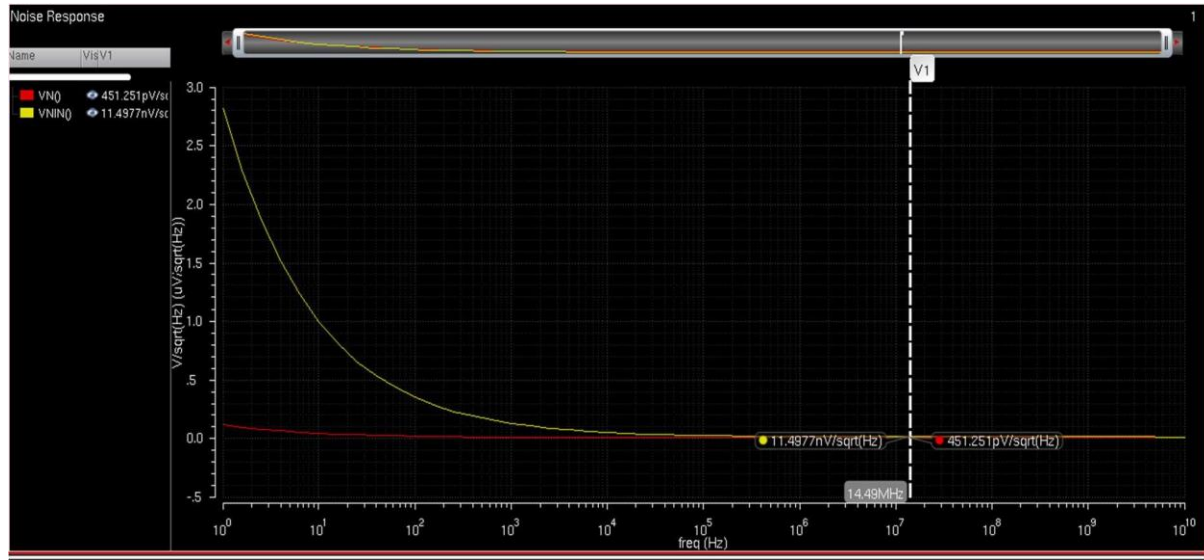f. NOISE

Input and output Noise is simulated in the following plot



CONCLUSIONS

<u>For $g_m = 20 \text{ mS}$</u>	<u>GAIN</u>	<u>BANDWIDTH</u>	<u>POWER</u>	<u>AREA</u>	<u>LINEARITY</u>
By varying I_D , $I_D = 1.90717 \text{ mA}$	21.8965 dB = 12.44	48.7616 MHz	2.262 mW	405.72 x 10^{-12} m^2	$HD_3 = 14.108 \%$
By varying V_{GS} , $V_{GS} = 0.64983 \text{ V}$	19.1071 dB = 9.023	67.192 MHz	1.804 mW	405.72 x 10^{-12} m^2	$HD_3 = 13.294 \%$
By varying W , $W = 17$	32.8557 dB =	13.8409 MHz	8.76 mW	299.8 x 10^{-12} m^2	$HD_3 = 15.1897 \%$

1. For a fixed g_m , increment in the no. of fingers and thus, the width of the MOSFET will decrease the r_0 and that will decrease the gain while decrease in the no. of fingers will reduce the Bandwidth but increase the gain.
2. $\frac{gm}{ID}$, gain and V_{GS} have a straight inter-dependency with each other for a given Gain-Bandwidth Product.
3. The circuit will work as an amplifier only for specific a range of V_{GS} as well as C_L .
4. The difference between Weak Inversion V_{GS} and strong Inversion V_{GS} is purely technology dependant and is same for a given nm-technology.